


7. Resistors in Series.

Resistors are said to be connected in "**Series**", when they are daisy chained together in a single line. Since all the current flowing through the first resistor has no other way to go it must also pass through the second resistor and the third and so on. Then, resistors in series have a **Common Current** flowing through them as the current that flows through one resistor must also flow through the others as it can only take one path. Then the amount of current that flows through a set of resistors in series is the same at all points in a series circuit. For example:

$$I_{R1} = I_{R2} = I_{R3} = I_{AB} = 1\text{mA}$$

In the following example the resistors R_1 , R_2 and R_3 are all connected together in series between points A and B.

Series Resistor Circuit

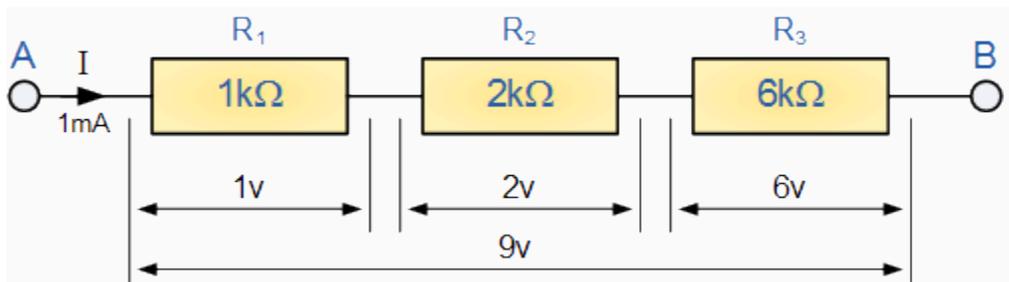


As the resistors are connected together in series the same current passes through each resistor in the chain and the total resistance, R_T of the circuit must be **equal** to the sum of all the individual resistors added together. That is

$$R_T = R_1 + R_2 + R_3$$

and by taking the individual values of the resistors in our simple example above, the total equivalent resistance, R_{EQ} is therefore given as:
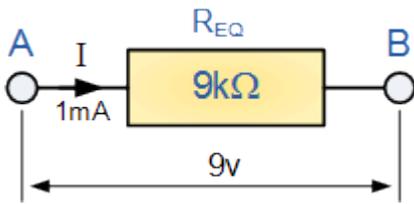
$$R_{EQ} = R_1 + R_2 + R_3 = 1\text{k}\Omega + 2\text{k}\Omega + 6\text{k}\Omega = 9\text{k}\Omega$$



So we can replace all three individual resistors above with just one single equivalent resistor which will have a value of $9k\Omega$.

Where four, five or even more resistors are all connected together in a series circuit, the total or equivalent resistance of the circuit, R_T would still be the sum of all the individual resistors connected together and the more resistors added to the series, the greater the equivalent resistance (no matter what their value). This total resistance is generally known as the **Equivalent Resistance** and can be defined as; "a single value of resistance that can replace any number of resistors in series without altering the values of the current or the voltage in the circuit". Then the equation given for calculating total resistance of the circuit when connecting together resistors in series is given as:

Series Resistor Equation

$$R_{total} = R_1 + R_2 + R_3 + \dots R_n \text{ etc.}$$

Note then that the total or equivalent resistance, R_T has the same effect on the circuit as the original combination of resistors as it is the algebraic sum of the individual resistances. One important point to remember about resistors in series circuits, the total resistance (R_T) of any two or more resistors connected together in series will always be **GREATER** than the value of the largest resistor in the chain and in our example above $R_T = 9k\Omega$ were as the largest value resistor is only $6k\Omega$.

Series Resistor Voltage

The voltage across each resistor connected in series follows different rules to that of the series current. We know from the above circuit that the total supply voltage across the resistors is equal to the sum of the potential differences across R_1 , R_2 and R_3 , $V_{AB} = V_{R1} + V_{R2} + V_{R3} = 9V$.

Using **Ohm's Law**, the voltage across the individual resistors can be calculated as:

$$\text{Voltage across } R_1 = IR_1 = 1mA \times 1k\Omega = 1V$$

$$\text{Voltage across } R_2 = IR_2 = 1mA \times 2k\Omega = 2V$$

$$\text{Voltage across } R_3 = IR_3 = 1mA \times 6k\Omega = 6V$$

giving a total voltage V_{AB} of $(1V + 2V + 6V) = 9V$ which is equal to the value of the supply voltage. Then the sum of the potential differences across the resistors is equal to the total potential difference across the combination and in our example this is $9V$.

The equation given for calculating the total voltage in a series circuit which is the sum of all the individual voltages added together is given as:


$$R_{\text{Total}} = V_{R1} + V_{R2} + V_{R3} + \dots + V_N$$

Then series resistor networks can also be thought of as "voltage dividers" and a series resistor circuit having N resistive components will have N -different voltages across it while maintaining a common current.

By using **Ohm's Law**, either the voltage, current or resistance of any series connected circuit can easily be found and resistor of a series circuit can be interchanged without affecting the total resistance, current, or power to each resistor.

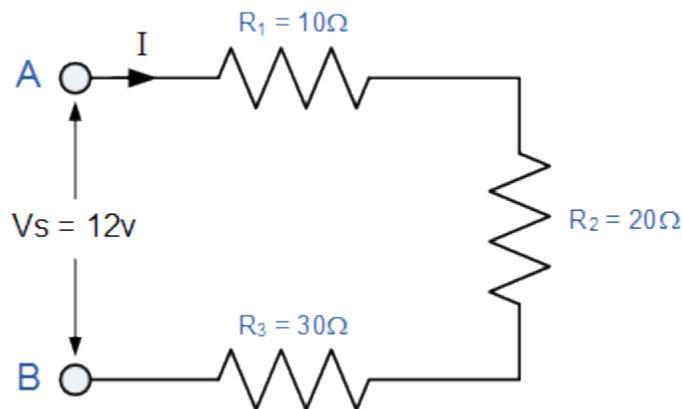Example No1

Calculate the equivalent resistance, series current, voltage drop and power for each resistor of the following resistors in series circuit.



All the data can be found by using **Ohm's Law**, and to make life a little easier we can present this data in tabular form.

Resistance	Current	Voltage	Power
$R_1 = 10\Omega$	$I_1 = 200\text{mA}$	$V_1 = 2\text{V}$	$P_1 = 0.4\text{W}$
$R_2 = 20\Omega$	$I_2 = 200\text{mA}$	$V_2 = 4\text{V}$	$P_2 = 0.8\text{W}$
$R_3 = 30\Omega$	$I_3 = 200\text{mA}$	$V_3 = 6\text{V}$	$P_3 = 1.2\text{W}$

$$R_T = 60\Omega$$

$$I_T = 200\text{mA}$$

$$V_S = 12\text{V}$$

$$P_T = 2.4\text{W}$$


The Potential Divider Circuit

Connecting resistors in series like this across a single DC supply voltage has one major advantage, different voltages appear across each resistor with the amount of voltage being determined by the resistors value only because as we now know, the current through a series circuit is common. This ability to generate different voltages produces a circuit called a **Potential or Voltage Divider Network**.

The series circuit shown above is a simple potential divider where three voltages 1V, 2V and 6V are produced from a single 9V supply. **Kirchoff's voltage laws** states that "the supply voltage in a closed circuit is equal to the sum of all the voltage drops (IR) around the circuit" and this can be used to good effect as this allows us to determine the voltage levels of a circuit without first finding the current.

The basic circuit for a potential divider network (also known as a voltage divider) for resistors in series is shown below.

Potential Divider Network

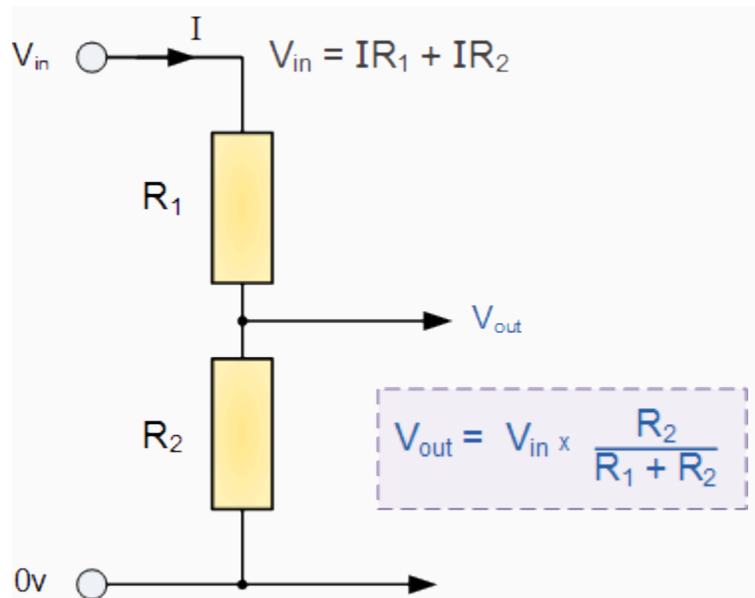

In this circuit the two resistors are connected in series across V_{in} , which is the power supply voltage connected to the resistor, R_1 , where the output voltage V_{out} is the voltage across the resistor R_2 which is given by the formula. If more resistors are connected in series to the circuit then different voltages will appear across each resistor with regards to their

individual resistance R (Ohms law $I \times R$) providing different voltage points from a single supply. However, care must be taken when using this type of network as the impedance of any load connected to it can affect the output voltage. For example,


Suppose you only have a 12V DC supply and your circuit which has an impedance of 50Ω requires a 6V supply. Connecting two equal value resistors, of say 50Ω each, together as a potential divider network across the 12V will do this very nicely until you connect your load circuit to the network. This is demonstrated below.

Example No2

Calculate the voltage across X and Y.

a) Without R_L connected

b) With R_L connected

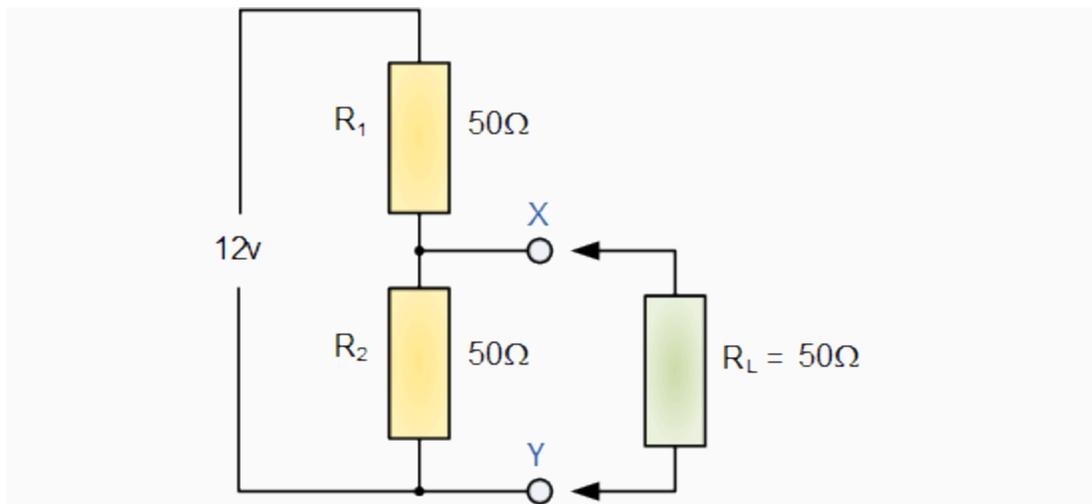

a) Without R_L connected

$$R_{X-Y} = 50\Omega$$

$$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2}$$

$$V_{out} = 12v \times \frac{50}{50 + 50} = 6.0v$$

b) With R_L connected

$$R_{X-Y} = 25\Omega \text{ (Resistors in Parallel)}$$

$$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2}$$

$$V_{out} = 12v \times \frac{25}{50 + 25} = 4.0v$$

As you can see from above, the output voltage V_{out} without the load resistor connected gives us the required output voltage

of 6V but the same output voltage at V_{out} when the load is connected drops to only 4V, (**Resistors in Parallel**). Then the output voltage V_{out} is determined by the ratio of V_1 to V_2 with the effect of reducing the signal or voltage level being known as **Attenuation** so care must be taken when using a potential divider networks. The higher the load impedance the less is the loading effect on the output.

A variable resistor, potentiometer or pot as it is more commonly called, is a good example of a multi-resistor potential divider within a single package as it can be thought of as thousands of mini-resistors in series. Here a fixed voltage is applied across the two outer fixed connections and the variable output voltage is taken from the wiper terminal. Multi-turn pots allow for a more accurate output voltage control.

Resistors in Series Applications

We have seen that resistors in series can be used to produce different voltages across themselves and this type of resistor network is very useful for producing a voltage divider network. If we replace one of the resistors in the voltage divider circuit above with a **Sensor** such as a thermistor, light dependant resistor (LDR) or even a switch, we can convert an analogue quantity being sensed into a suitable electrical signal which is capable of being measured.

Ref: http://www.electronics-tutorials.ws/resistor/res_3.html

23 March 2014

Benny haastrup